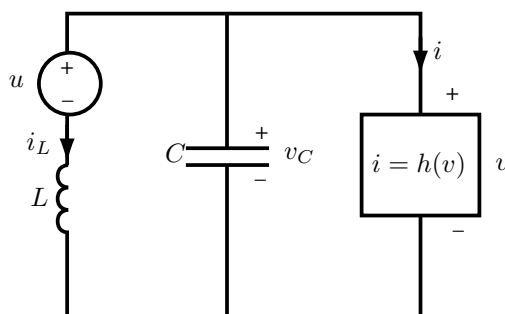


ECE311S: Dynamic Systems and Control


Problem Set 1

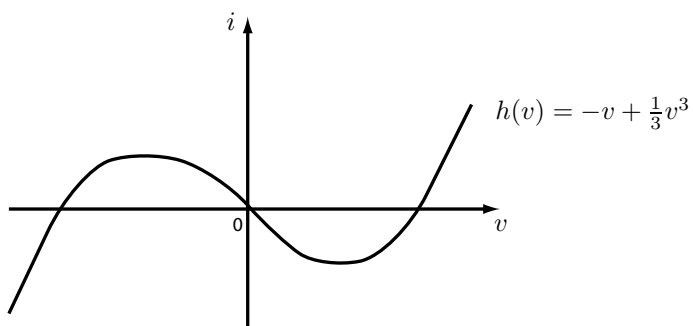Problem 1

The controlled Van der Pol oscillator has the circuit diagram shown below.




The output of the system is the voltage across the capacitor, v_C . The nonlinear element of the circuit has a characteristic $i = h(v)$, depicted below, with $h(v) = -v + \frac{1}{3}v^3$.



- (i) Write the mathematical model of the system in terms of v_C , i_L , and u .
- (ii) Letting $x_1 = i_L$ and $x_2 = v_C$, write the state-space model of the system.

Problem 2


Write the equations of motion of the system below, where x_1 and x_2 represent deviations from the equilibrium position.

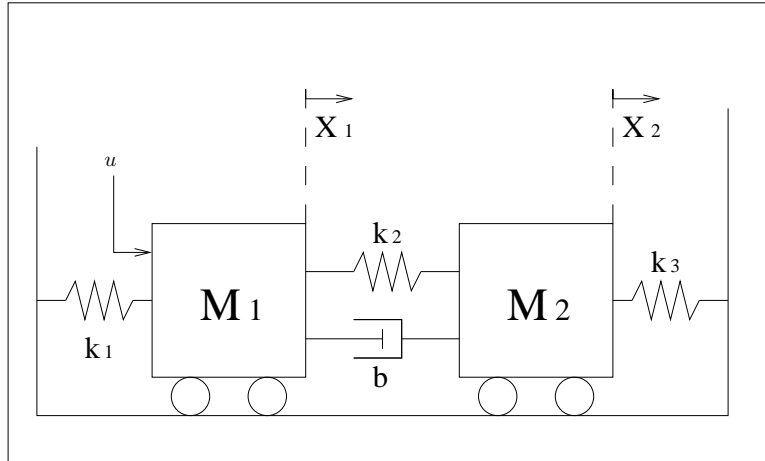

Problem 3



Write the equations of motion of the system below.

- Suppose the center of gravity of the pendulum rod is at its geometric center.
- Neglect the moment of inertia of the wheels.

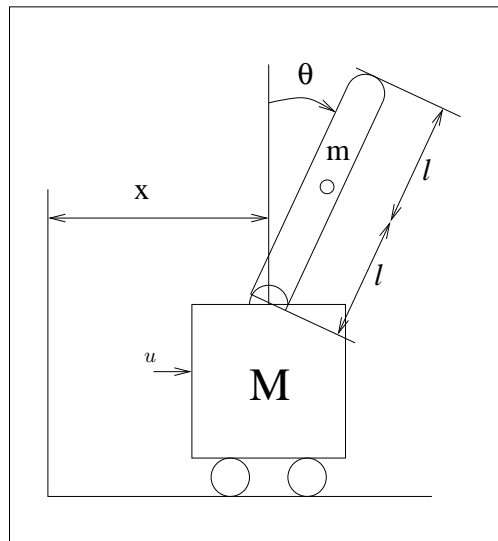

Problem 4

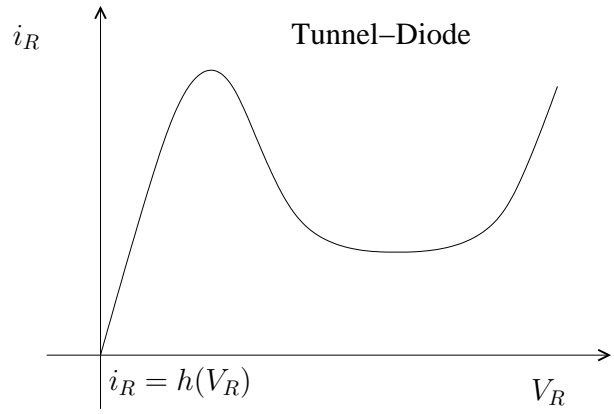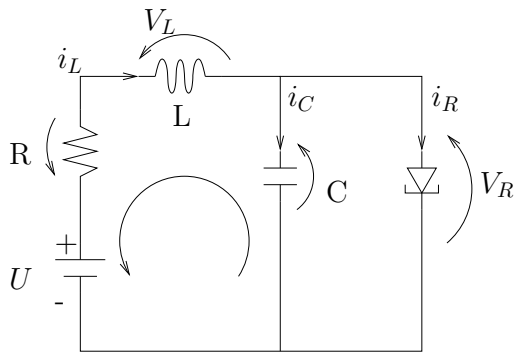1. Write the equations of the circuit below.
2. Write the state-variable model of the system.
3. Find the equilibria holding u constant.



The diode has a nonlinear characteristic